

# **UNIT 1: DC CIRCUITS**



Lecture 1

Prepared By:

Krishan Arora

Assistant Professor and Head

# Electrical Circuit

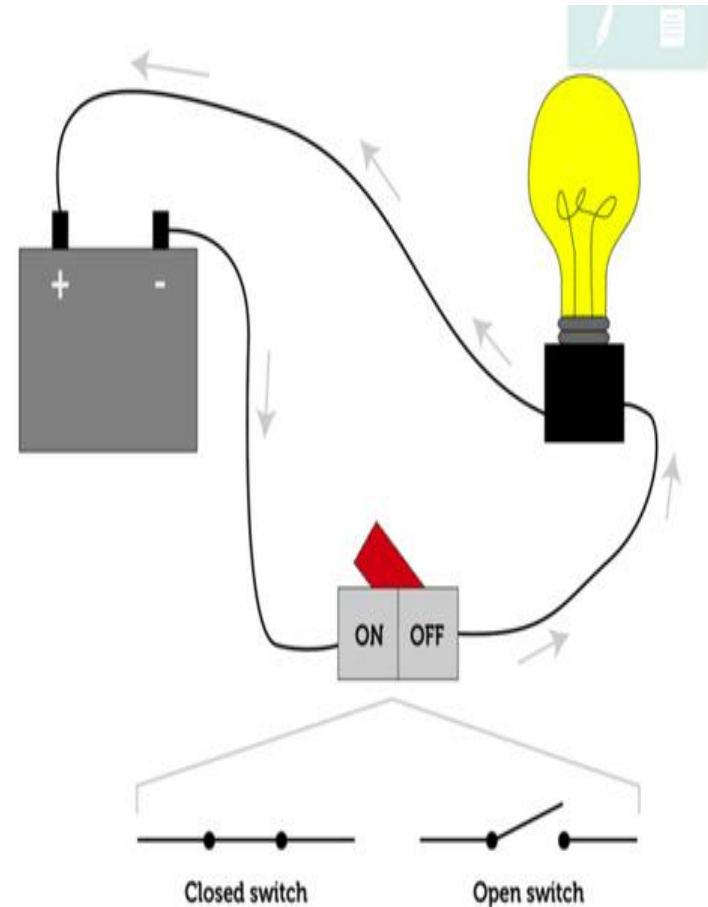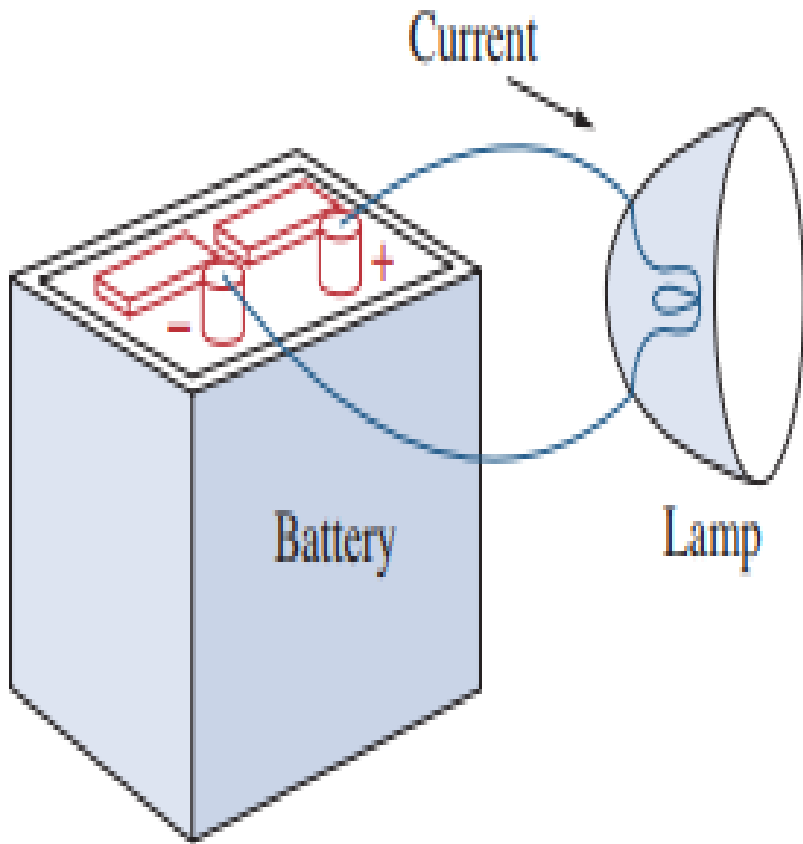

# Charge and Current

- **Charge:** Charge is an electrical property of the atomic particles of a matter.

S.I Unit: Coulomb (C)

Symbol: Q


- **Current:** Rate of change of charge.

OR

Continuous flow of electrons in an electrical circuit.

S.I Unit: Ampere (A)

Symbol: I

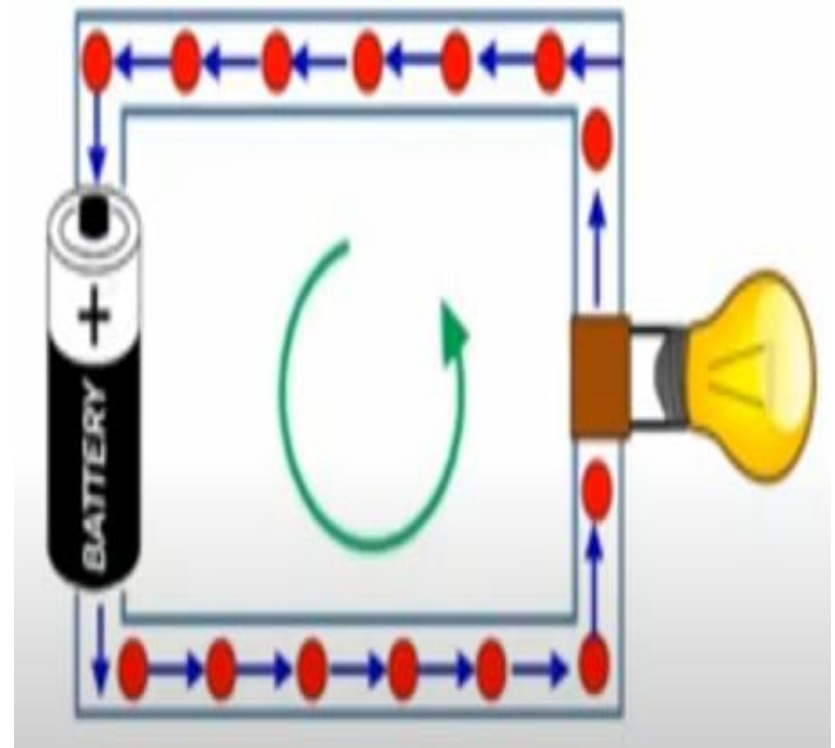

# Charge and Current

- Mathematically,

$$I = \frac{dQ}{dt} \text{ or } Q = \int_{t_0}^t I \cdot dt$$

Or, in simple terms:

$$I = \frac{Q}{T}$$

So, 1 Ampere = 1 coulomb/ 1 second.

# QUICK QUIZ (Poll 1)

1 Coulomb is same as:

- A. Watt /sec
- B. Ampere/sec
- C. Joule-sec
- D. Ampere-sec

# QUICK QUIZ (Poll 2)

*Example:* The total charge entering a terminal is given by  $q(t)=5t\sin 4\pi t$  mC. Calculate the current at  $t=0.5$ s

**A.31.42A**

**B.31.42mA**

**C.62.8mA**

**D.62.8A**


# Explanation

$$i(t) = \frac{dq(t)}{dt} = \frac{d}{dt}(5t \sin 4\pi t) = (5 \sin 4\pi t + 20\pi t \cos 4\pi t) \text{mA}$$

$$i(0.5) = 5 \sin 2\pi + 10\pi \cos 2\pi = 31.42 \text{mA}$$
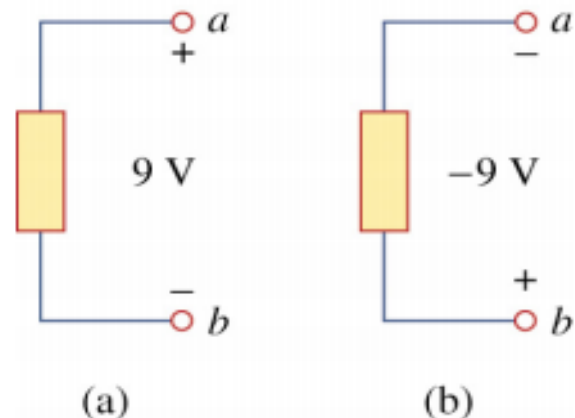
# Voltage

- To move an electron from point  $a$  to point  $b$ , external electromotive force (emf), typically a battery, is needed
- The voltage  $v_{ab}$  between two points  $a$  and  $b$  is the energy needed to move a unit charge from  $a$  to  $b$
- Mathematically,  $v_{ab} \triangleq \frac{dw}{dq}$
- 1 volt = 1 joule / coulomb
- Two equivalent representations:
  - Point  $a$  is  $v_{ab}=+9\text{V}$  above point  $b$
  - Point  $b$  is  $v_{ba}=-9\text{V}$  above point  $a$
  - In general,  $v_{ab} = -v_{ba}$





# Power and Energy

- **Power:** Rate at which the work is done.

OR

Time rate of absorbing or supplying energy

S.I Unit: Watts (W)

Symbol: P

Mathematically,

$$P = \frac{dW}{dt} = \frac{dW}{dq} \cdot \frac{dq}{dt} = V \cdot I$$

Implies,  $P = V \cdot I$

# Power and Energy

- **Energy:** Capacity of doing work.  
S.I Unit: Joules(J)  
Symbol: E

# QUICK QUIZ (Poll 3)

Calculate the current ratings of 100 Watt incandescent bulb and 15 Watt LED lamp operated with the domestic supply of 220 Volt?

- A. Bulb = 0.068 A and LED = 0.45 A
- B. Bulb = 0.45 A and LED = 0.068 A
- C. Bulb = 0.50 A and LED = 0.068 A
- D. Bulb = 0.50 and LED = 0.68 A

# QUICK QUIZ (Poll 4)

From the previous question, it can be inferred that:

- A. LED consumes 5 times more current than Bulb.
- B. Bulb consumes 5 times more current than LED..
- C. LED consumes 6.6 times more current than Bulb.
- D. Bulb consumes 6.6 times more current than LED.

# Network Components

- **Passive elements:** not capable of generating energy
  - e.g., resistors, capacitors, and inductors
- **Active elements:** capable of generating energy
  - e.g., generators, batteries, and operational amplifiers

Active

Battery

Transistor, Op-amp, etc

Passive

Resistance (R)

Capacitance (C)


Inductance (L)

# Resistance

- **Resistance:** It is an opposition to the flow of current.

S.I Unit: Ohm ( $\Omega$ )

Symbol: R

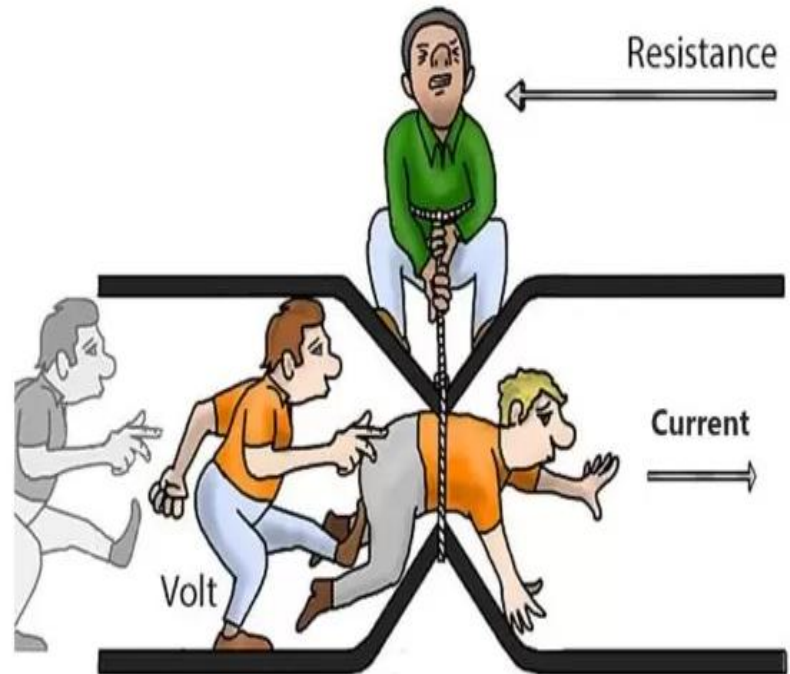

# Capacitance


- **Capacitance** is the ability of a device to store electrical energy in an electrostatic field.
- A **capacitor** is a device that stores energy in the form of an electrical field..
- A capacitor is made of two conductors separated by a dielectric.

S.I Unit: Farad (F)

Symbol: C

## Two important Properties:

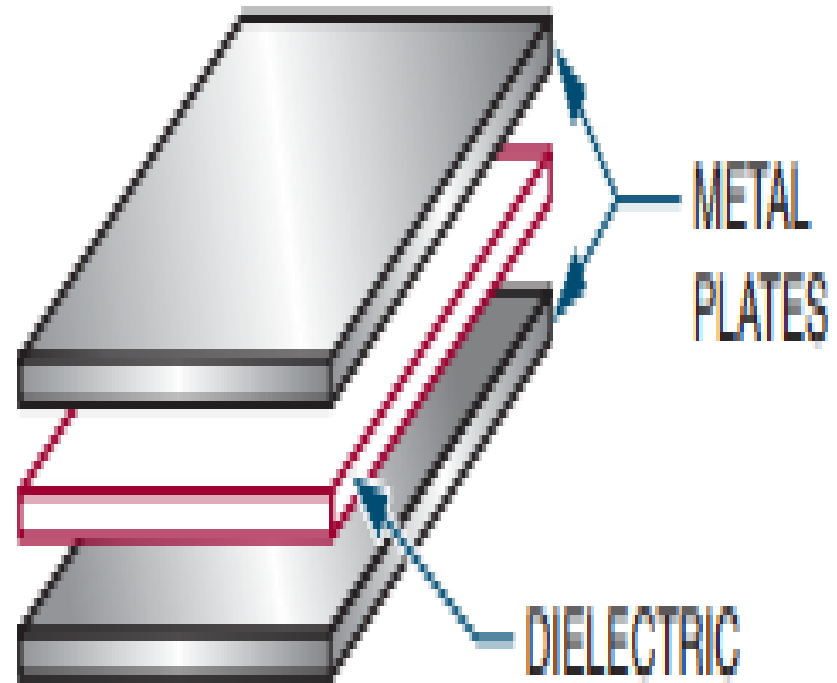1. No current flows through the capacitor, if the voltage remains constant.
2. Voltage across a capacitor cannot change instantaneously.



# Inductance


- **Inductance** is the characteristic of an electrical conductor that opposes a change in current flow.
- An **inductor** is a device that stores energy in a magnetic field.
- When a current flows through a conductor, magnetic field builds up around the conductor. This field contains energy and is the foundation for inductance

S.I Unit: Henry (H)

Symbol: L

## Two important Properties:

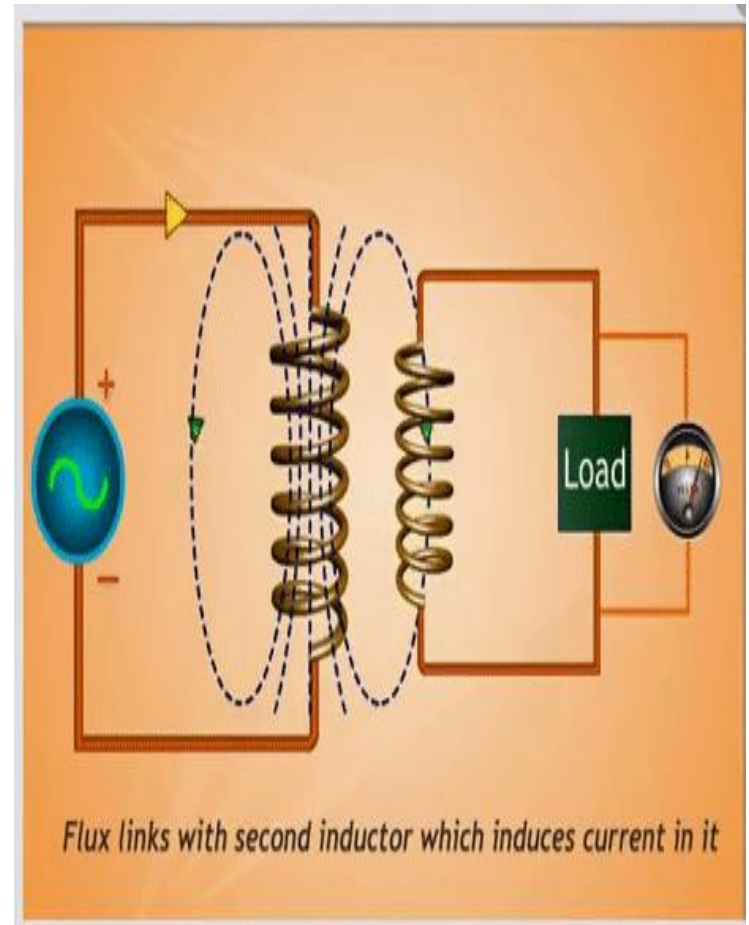1. No voltage appears across an inductor, if the current through it remains constant.
2. The current through an inductor cannot change instantaneously.






# Capacitance and Inductance

- $Q = CV$

- $I = \frac{dQ}{dt} = \frac{d CV}{dt} = C \frac{dV}{dt}$

- $E = \frac{1}{2} CV^2$


- $C = \frac{A\epsilon}{d}$

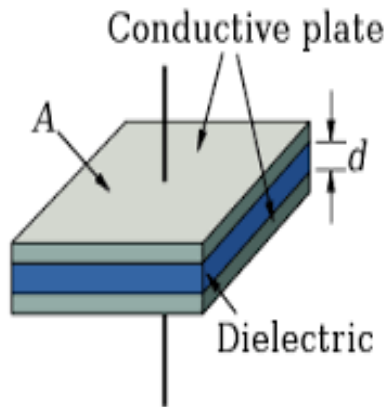

- $V = L \frac{dI}{dt}$

- $E = \frac{1}{2} LI^2$

- $L = \frac{\mu N^2 A}{l}$

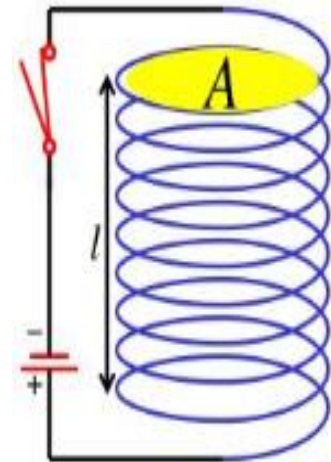

# QUICK QUIZ (Poll 5)

Identify the passive element

- A. Battery
- B. Transformer
- C. Transistor
- D. OP-amp
- E. None of these

# QUICK QUIZ (Poll 6)

Find the value of capacitance if the value of voltage increases linearly from 0 to 100 V in 0.1 s causing a current flow of 5 mA?

- A. 10  $\mu\text{F}$
- B. 5 F
- C. 10 F
- D. 5  $\mu\text{F}$