

# **ECE132: Basic Electrical and Electronics Engineering Lab**

**Experiment 1:** The verification of Kirchhoff's voltage law and Kirchhoff's current law

# Introduction

In complex circuits such as bridge or T networks, we can not simply use Ohm's Law alone to find the voltages or currents circulating within the circuit. For these types of calculations we need certain rules which allow us to obtain the circuit equations and for this we can use **Kirchhoffs Circuit Law**.


It states that, "In any network of conductors, the algebraic sum of currents meeting at a point (or junction) is zero".

In other words the algebraic sum of ALL the currents entering and leaving a node must be equal to zero,  $I(\text{exiting}) + I(\text{entering}) = 0$

# Kirchhoffs Circuit Law
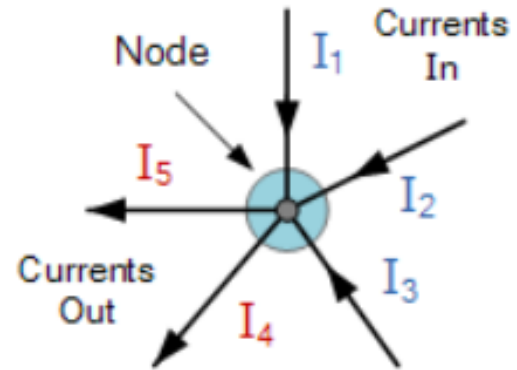
## Kirchhoffs Current Law

Currents Entering the Node  
Equals  
Currents Leaving the Node




$$I_1 + I_2 + I_3 + (-I_4 + -I_5) = 0$$

# Kirchhoffs Circuit Law

Using **Kirchhoffs Current Law, KCL** the equations are given as:

At node A :  $I_1 + I_2 = I_3$

At node B :  $I_3 = I_1 + I_2$

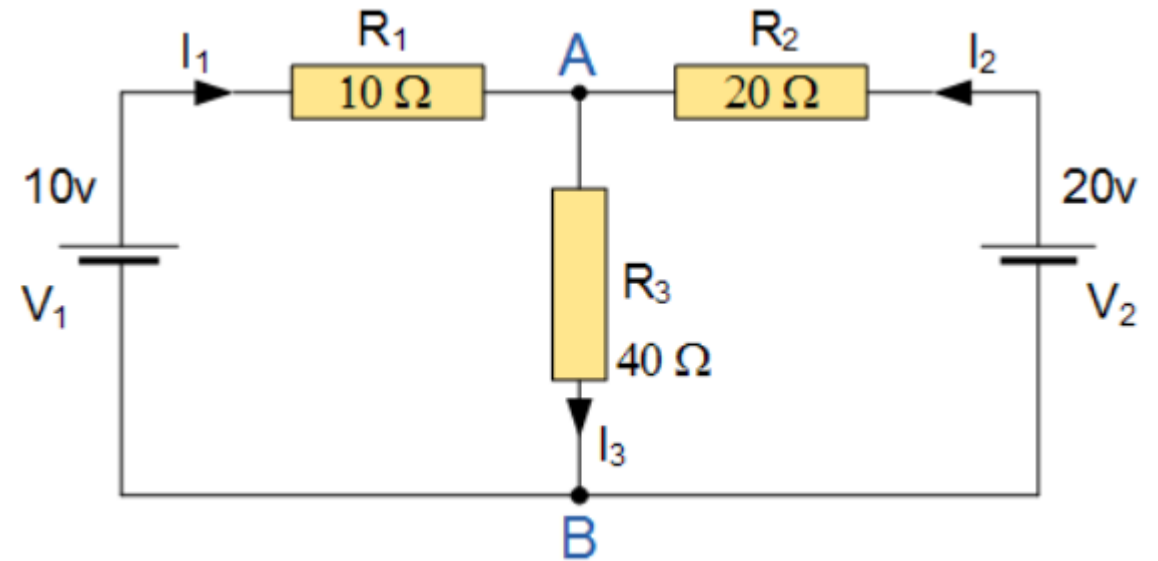

# Kirchhoffs Circuit Law

$$I_1 + I_2 = I_3$$

$$I_1 = \frac{V_1 - V_A}{R_1} \quad I_3 = \frac{V_A - V_3}{R_3}$$

$$I_2 = \frac{V_2 - V_A}{R_2} \quad \text{Assume } V_3 = 0$$

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} = \frac{V_A}{R_3}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} - V_A \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] = \frac{V_A}{R_3}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_A}{R_3} + V_A \left[ \frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = V_A \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = V_A \left[ \frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_2 R_3} \right]$$

$$\frac{10}{10} + \frac{20}{20} = V_A \left[ \frac{800 + 400 + 200}{8000} \right]$$

$$2 \times \frac{8000}{7400} = 11.428 = V_A$$

$$I_1 = \frac{10 - 11.428}{10} = -0.1428$$

$$I_2 = \frac{20 - 11.428}{20} = 0.4286$$

$$I_3 = \frac{11.428}{40} = 0.2857$$

# Kirchhoffs Circuit Law

Using **Kirchhoffs Current Law, KCL** the equations are given as:


$$\text{At node A : } I_1 + I_2 = I_3$$

$$\text{At node B : } I_3 = I_1 + I_2$$

$$I_1 = -0.1428 \text{ amp}$$


$$I_2 = 0.4286 \text{ amp}$$

$$I_3 = 0.2857 \text{ amp}$$

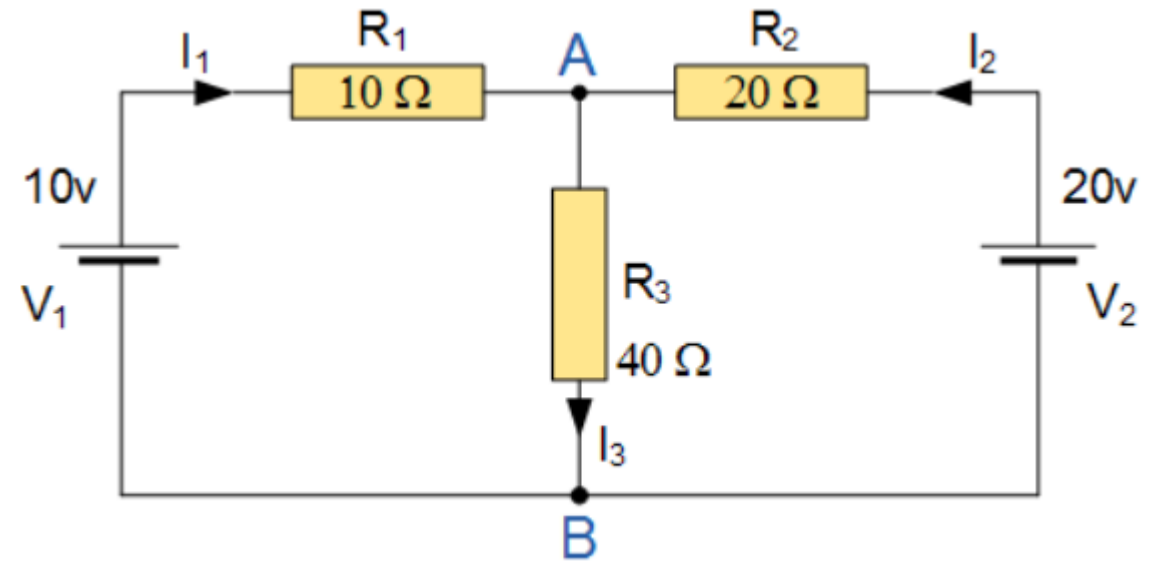
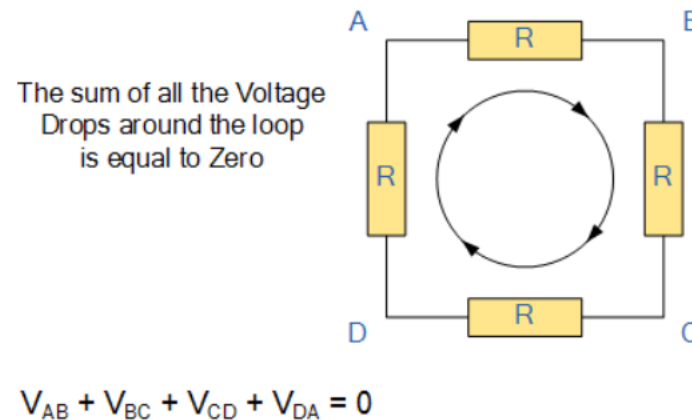
# Kirchhoffs Voltage Law


**Kirchhoffs Voltage Law** or KVL, states that *“in any closed loop network, the total voltage around the loop is equal to the sum of all the voltage drops within the same loop”* which is also equal to zero. In other words the algebraic sum of all voltages within the loop must be equal to zero.


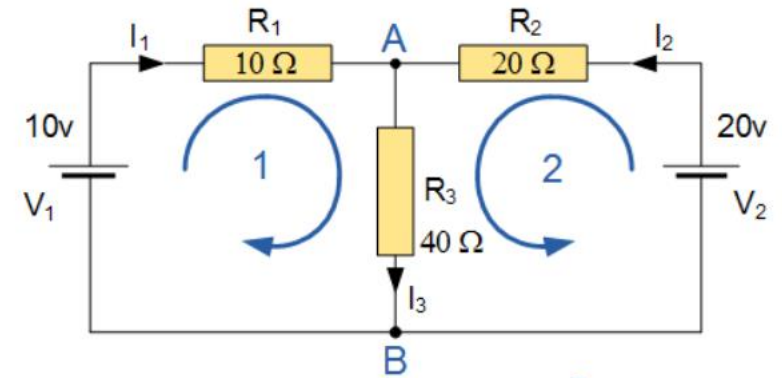
# Kirchhoffs Voltage Law

Using **Kirchhoffs Voltage Law, KVL** the equations are given as:

- Loop 1 is given as :  $10 = R_1 I_1 + R_3 I_3 = 10I_1 + 40I_3$
- Loop 2 is given as :  $20 = R_2 I_2 + R_3 I_3 = 20I_2 + 40I_3$





# Kirchhoffs Voltage Law


$$\begin{aligned}10 &= R_1 I_1 + R_6 I_3 \\10 &= 10 I_1 + 40 I_3 \quad (I_3 = I_1 + I_2) \\10 &= 50 I_1 + 40 I_2 \quad \text{--- (1)} \\20 &= R_2 I_2 + R_3 I_3 \\20 &= 20 I_2 + 40 I_3 \quad (I_3 = I_1 + I_2) \\20 &= 60 I_2 + 40 I_1 \quad \text{--- (2)}\end{aligned}$$
$$\begin{aligned}10 &= 50 I_1 + 40 I_2 & \times 60 \\20 &= 40 I_1 + 60 I_2 & \times 40\end{aligned}$$
$$\begin{aligned}600 &= 3000 I_1 + 2400 I_2 \\800 &= 1600 I_1 + 2400 I_2 \\-200 &= 1400 I_1 \quad \div 0\end{aligned}$$
$$\begin{aligned}-200 &= I_1 \quad \div 1400 \\I_1 &= -0.1428 \\I_2 &= 0.4286 \\I_3 &= 0.2857\end{aligned}$$
$$\begin{aligned}V_{R1} &= R_1 I_1 = -1.428 \\V_{R3} &= R_3 I_3 = 11.428 \\V_{R4} &= R_4 I_2 = 8.572\end{aligned}$$

# Kirchhoffs Voltage Law

Using **Kirchhoffs Voltage Law, KVL** the equations are given as:


- Loop 1 is given as :  $10 = R_1 I_1 + R_3 I_3 = 10I_1 + 40I_3$
- Loop 2 is given as :  $20 = R_2 I_2 + R_3 I_3 = 20I_2 + 40I_3$

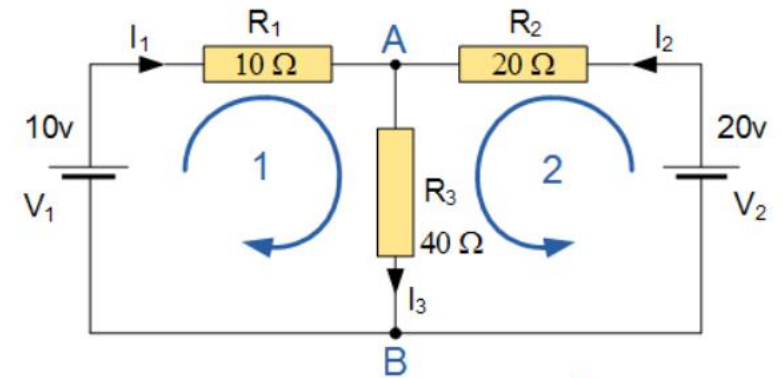- $VR1 = -1.428$
- $VR2 = 8.572$
- $VR3 = 11.428$



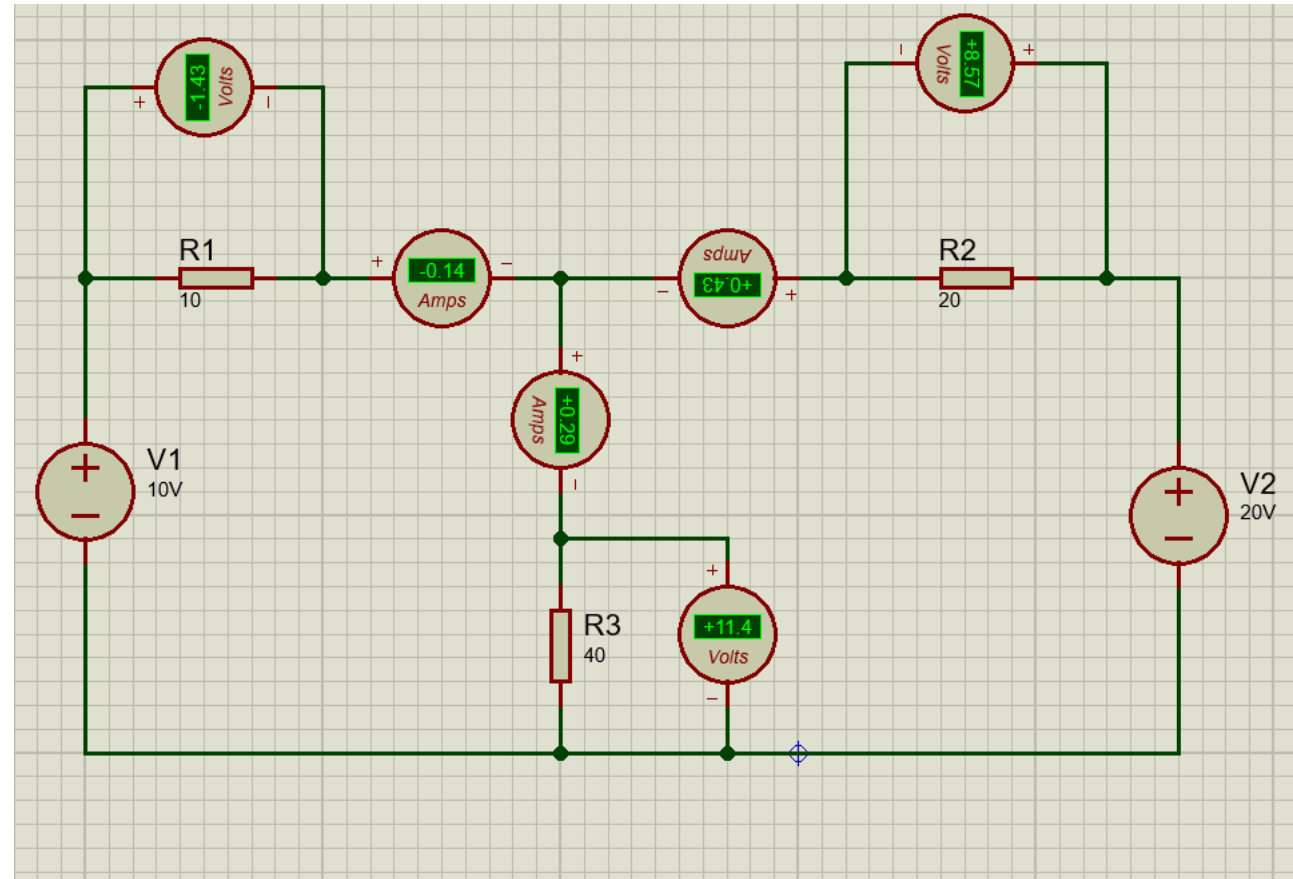
# Let Verify using Proteus

- $I_1 = -0.1428$  amp
- $I_2 = 0.4286$  amp
- $I_3 = 0.2857$  amp
- $VR1 = -1.428$
- $VR2 = 8.572$
- $VR3 = 11.428$



# Problem to be solved

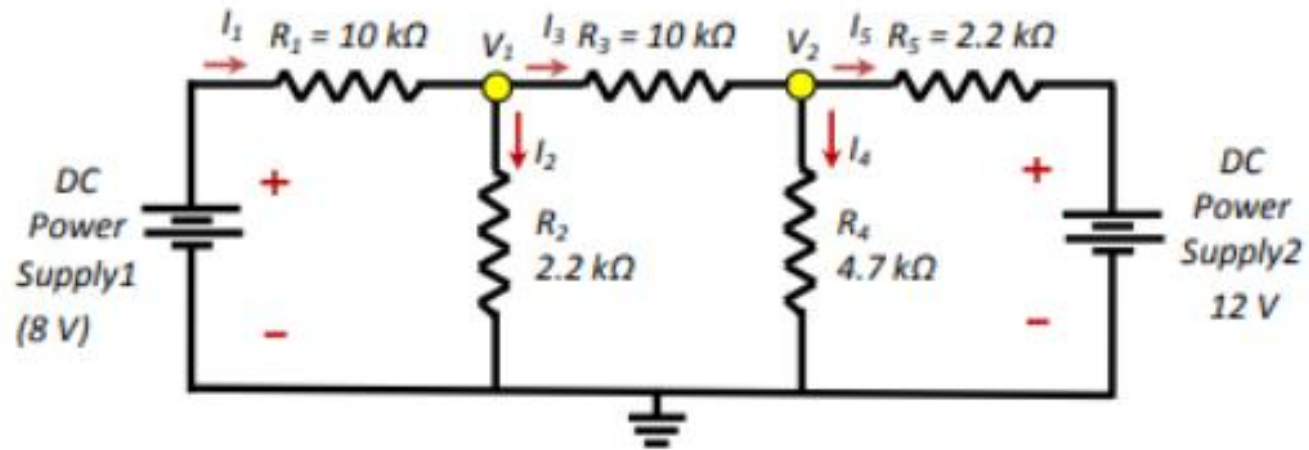

Thanks You