

## UNIT-II

# FUNDAMENTAL OF AC CIRCUITS

Lecture 12

Prepared By:

Krishan Arora

Assistant Professor and Head


# Inductors in an AC Circuit

Kirchhoff's loop rule can be applied and gives:

$$\Delta v + \Delta v_L = 0, \text{ or}$$

$$\Delta v - L \frac{di}{dt} = 0$$
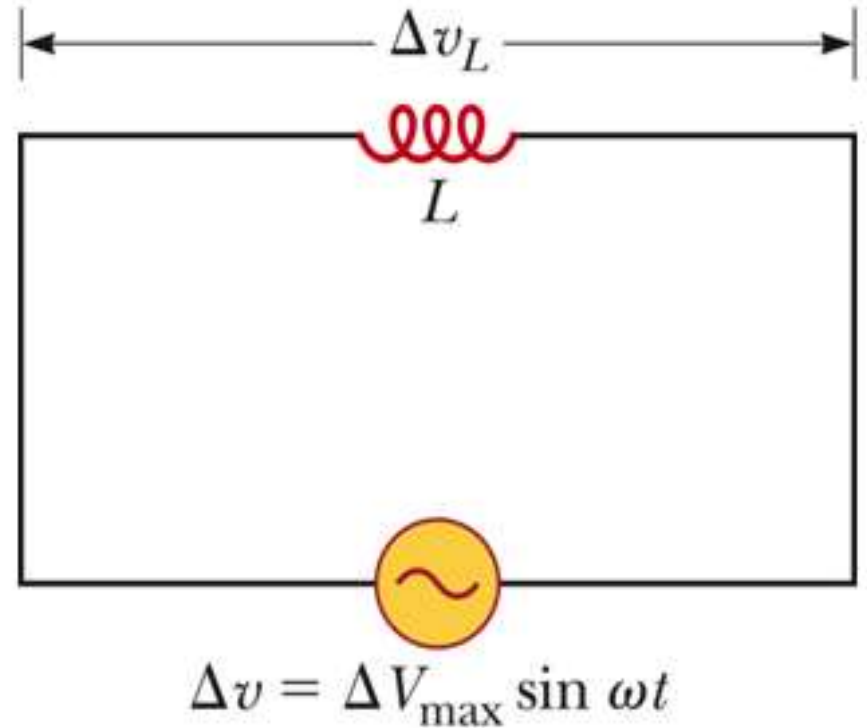
$$\Delta v = L \frac{di}{dt} = \Delta V_{\max} \sin \omega t$$



# Current in an Inductor

The equation obtained from Kirchhoff's loop rule can be solved for the current

$$i_L = \frac{\Delta V_{\max}}{L} \int \sin \omega t \, dt = -\frac{\Delta V_{\max}}{\omega L} \cos \omega t$$

$$i_L = \frac{\Delta V_{\max}}{\omega L} \sin\left(\omega t - \frac{\pi}{2}\right) \quad I_{\max} = \frac{\Delta V_{\max}}{\omega L}$$


This shows that the instantaneous current  $i_L$  in the inductor and the instantaneous voltage  $\Delta V_L$  across the inductor are out of phase by  $(\pi/2)$  rad =  $90^\circ$ .

# Phase Relationship of Inductors in an AC Circuit

The current is a maximum when the voltage across the inductor is zero.

- The current is momentarily not changing

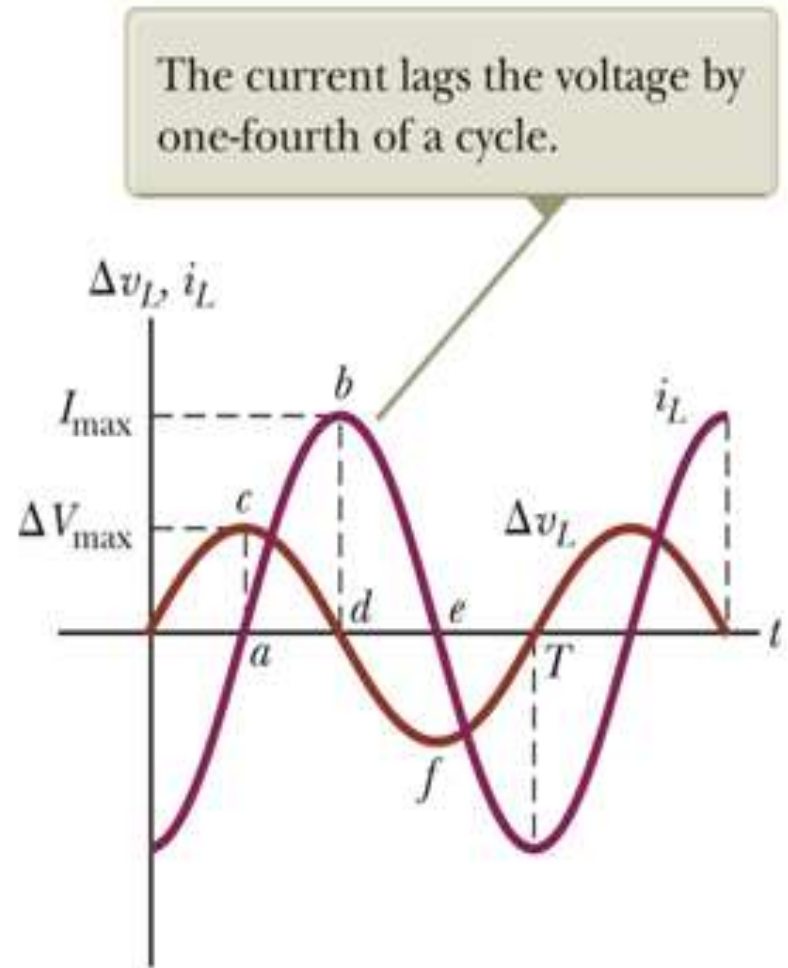For a sinusoidal applied voltage, the current in an inductor always lags behind the voltage across the inductor by  $90^\circ$  ( $\pi/2$ ).




# Phasor Diagram for an Inductor

The phasors are at  $90^\circ$  with respect to each other.

This represents the phase difference between the current and voltage.

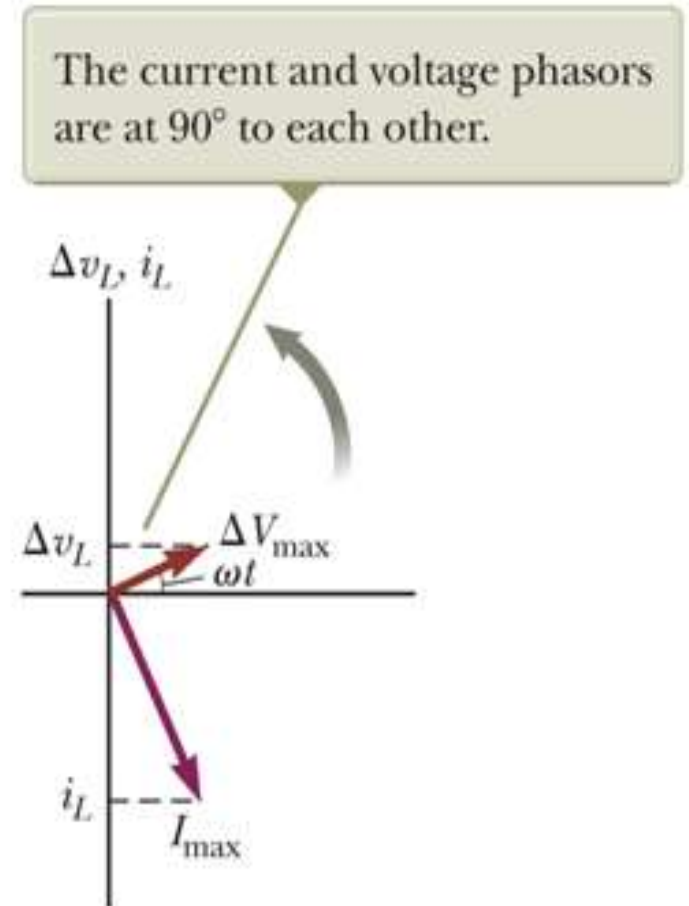Specifically, the current lags behind the voltage by  $90^\circ$ .



# Inductive Reactance

The factor  $\omega L$  has the same units as resistance and is related to current and voltage in the same way as resistance.

Because  $\omega L$  depends on the frequency, it reacts differently, in terms of offering resistance to current, for different frequencies.

The factor is the inductive reactance and is given by:

- $X_L = \omega L$

# Inductive Reactance, cont.

Current can be expressed in terms of the inductive reactance:

$$I_{\max} = \frac{\Delta V_{\max}}{X_L} \text{ or } I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{X_L}$$

As the frequency increases, the inductive reactance increases

- This is consistent with Faraday's Law:
  - The larger the rate of change of the current in the inductor, the larger the back emf, giving an increase in the reactance and a decrease in the current.

# Voltage Across the Inductor

The instantaneous voltage across the inductor is

$$\begin{aligned}\Delta v_L &= -L \frac{di}{dt} \\ &= -\Delta V_{\max} \sin \omega t \\ &= -I_{\max} X_L \sin \omega t\end{aligned}$$



# Quick Quiz (Poll 1)

- The two quantities are said to be in phase with each other when
  - a. the phase difference between two quantities is zero degree or radian
  - b. each of them pass through zero values at the same instant and rise in the same direction
  - c. each of them pass through zero values at the same instant but rises in the opposite directions
  - d. Both (a) or (b)

# Quick Quiz (Poll 2)

- The inductive reactance of a circuit .....  
with the increase in supply frequency
  - a. increases
  - b. decreases
  - c. remains unchanged
  - d. unpredictable

# Capacitors in an AC Circuit


The circuit contains a capacitor and an AC source.

Kirchhoff's loop rule gives:

$$\Delta v + \Delta v_C = 0 \text{ and so}$$

$$\Delta v = \Delta v_C = \Delta V_{\max} \sin \omega t$$

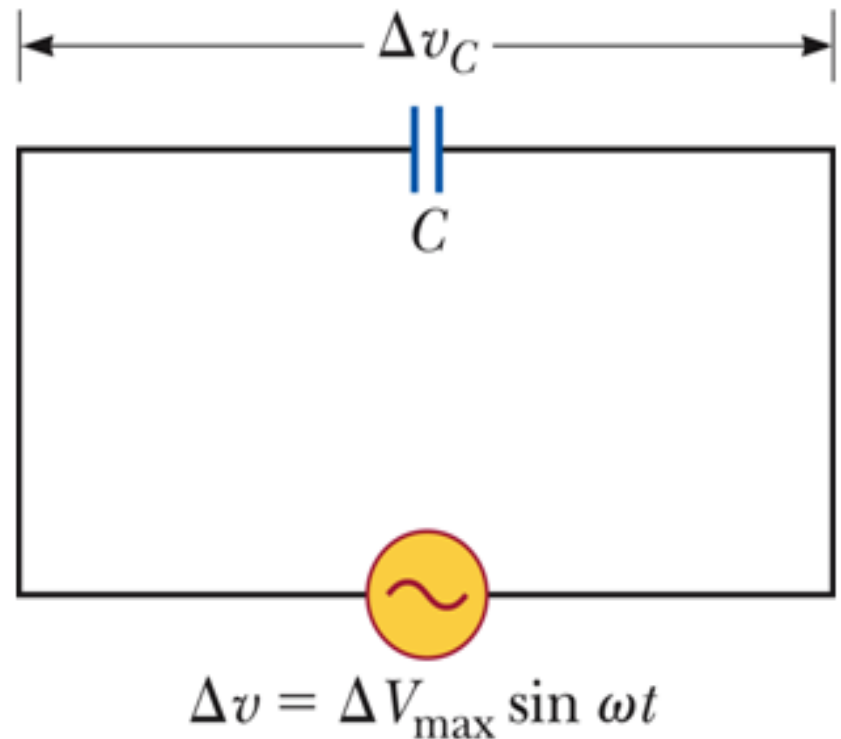- $\Delta v_C$  is the instantaneous voltage across the capacitor.



# Capacitors in an AC Circuit, cont.

The charge is  $q = C\Delta V_{\max} \sin \omega t$

The instantaneous current is given by

$$i_C = \frac{dq}{dt} = \omega C\Delta V_{\max} \cos \omega t$$


$$\text{or } i_C = \omega C\Delta V_{\max} \sin\left(\omega t + \frac{\pi}{2}\right)$$

The current is  $\pi/2$  rad =  $90^\circ$  out of phase with the voltage
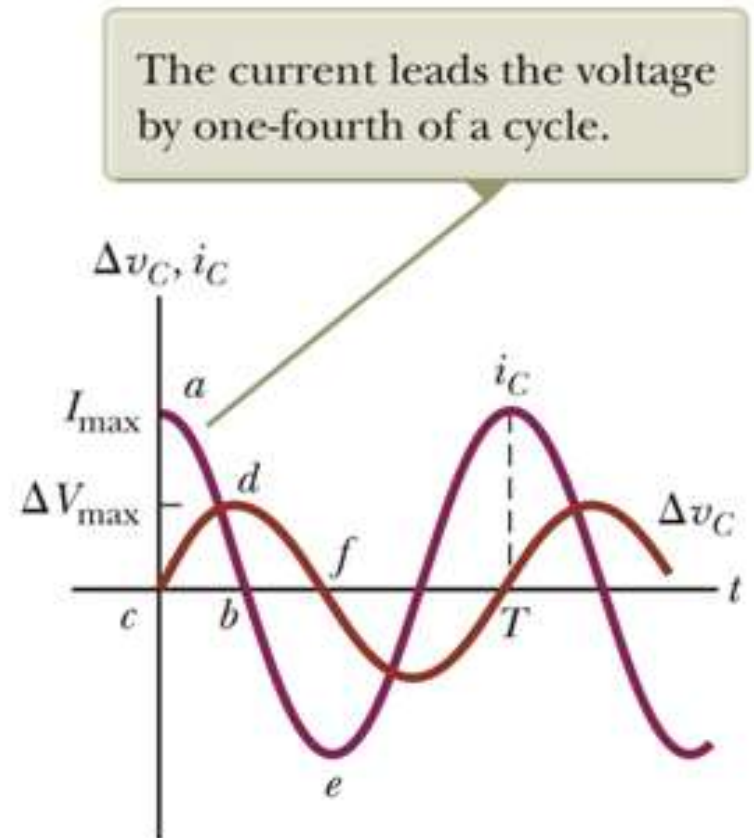
# More About Capacitors in an AC Circuit

The current reaches its maximum value one quarter of a cycle sooner than the voltage reaches its maximum value.


The current leads the voltage by  $90^\circ$ .


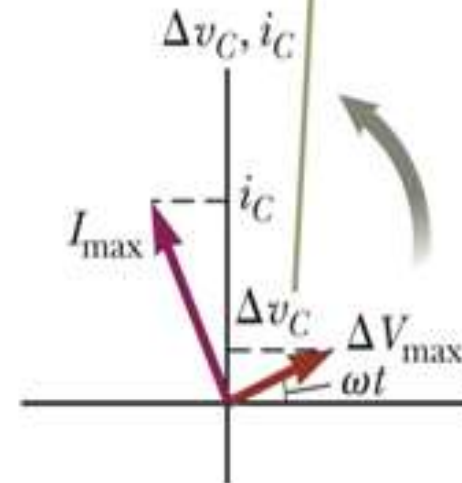
# Phasor Diagram for Capacitor

The phasor diagram shows that for a sinusoidally applied voltage, the current always leads the voltage across a capacitor by  $90^\circ$ .

The current and voltage phasors are at  $90^\circ$  to each other.



# Capacitive Reactance

The maximum current in the circuit occurs at  $\cos \omega t = 1$  which gives

$$I_{\max} = \omega C \Delta V_{\max} = \frac{\Delta V_{\max}}{(1/\omega C)}$$

The impeding effect of a capacitor on the current in an AC circuit is called the **capacitive reactance** and is given by

$$X_C \equiv \frac{1}{\omega C} \quad \text{which gives} \quad I_{\max} = \frac{\Delta V_{\max}}{X_C}$$

# Voltage Across a Capacitor

The instantaneous voltage across the capacitor can be written as  $\Delta v_C = \Delta V_{max} \sin \omega t = I_{max} X_C \sin \omega t$ .

As the frequency of the voltage source increases, the capacitive reactance decreases and the maximum current increases.

As the frequency approaches zero,  $X_C$  approaches infinity and the current approaches zero.

- This would act like a DC voltage and the capacitor would act as an open circuit.



# Quick Quiz (Poll 3)

- In a pure capacitive circuit, the current will
  - a. lag behind the voltage by 90 degree
  - b. lead behind the voltage by 90 degree
  - c. remains in phase with voltage
  - d. none of the above

# Quick Quiz (Poll 4)

- A phasor is a line which represents the
  - a. rms value and phase of an alternating quantity
  - b. average value and phase of an alternating quantity
  - c. magnitude and direction of an alternating quantity
  - d. none of the above